

## Form 4 Physics Midterm Exam: Electricity

### Section A: Multiple Choice Questions

**Instructions: Choose the most appropriate answer for each question.**

1. Which of the following statements about electric current is correct?
  - A. Electric current is the flow of protons.
  - B. Electric current is measured in joules.
  - C. Electric current flows from positive to negative.
  - D. Electric current depends only on resistance.
  
2. When resistors are connected in series, the total resistance:
  - A. Decreases
  - B. Increases
  - C. Remains the same
  - D. Becomes zero
  
3. What is the voltage across a 10-ohm resistor with a current of 2 amps flowing through it?
  - A. 5 V
  - B. 12 V
  - C. 20 V
  - D. 0.2 V
  
4. A 12 V battery is connected to a circuit with two resistors in parallel, 4 ohms each. What is the total current drawn from the battery?

- A. 1 A
- B. 2 A
- C. 3 A
- D. 4 A

5. Which of the following devices converts electrical energy into mechanical energy?

- A. Capacitor
- B. Resistor
- C. Electric motor
- D. Diode

### **Section B: Short Answer Questions**

Instructions: Answer all questions concisely and clearly.

6. Explain how Ohm's law is applied to calculate current in a circuit. Include an example calculation.

7. Define capacitance. How does the capacitance of a capacitor change if the distance between the plates is increased? Explain.

8. Describe how an ammeter is connected in a circuit to measure current. Include any precautions that should be taken.

### **Section C: Problem-solving Questions**

Instructions: Show all your work clearly and include units in your answers.

9. Calculate the total resistance of the following circuit:

![[Circuit Diagram]](image-link)

10. A 6 V battery is connected to charge a 100  $\mu\text{F}$  capacitor through a 500-ohm resistor. Calculate:

- a) The time constant of the circuit.
- b) The charge on the capacitor after 5 seconds of charging.

#### **Section D: Extended Response Question**

Instructions: Answer one question in detail.

11. Discuss the advantages and disadvantages of using parallel and series circuits in household electrical wiring.